



<http://www.autodesk.com/>
Featured Download Internet of Things Contest (/contest/iot2017/?utm_source=featurebar/)

Contests (/əˈkɒntɛst/)

Classes (classes)



(<http://www.autodesk.com/>)
Featured: Download

I Made it!

♥ Favorite


 Share

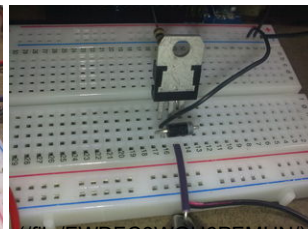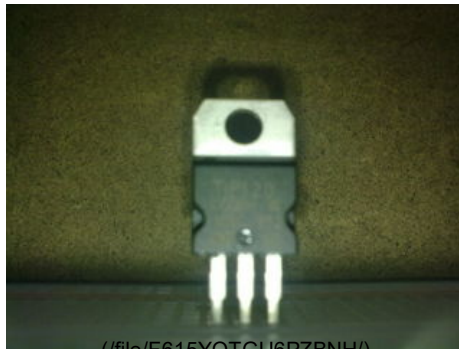3D Scanning Class (/class/3D-Scanning-Class/?utm_source=featurebar/)




Show All Items

 CC BY-NC-SA



Real IR Remote Control Design

TV-/)



(/id/Modify-The-HC-

05-Bluetooth-Module-Defaults-Using-A/)

Easy, Reversible Motor Control for Arduino (or any Microcontroller) ([id/Super-Easy-Reversible-Motor-Control-for-Arduino](#))

Hello again.

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

So you have a DC motor or lamp but no matter how you connect them to your Arduino they just won't work? Guess what, the Arduino is a brain that controls those power motors or lights you need for your next project. The Arduino is good at thinking but not for heavy lifting. Lazy lad.


Download

+ Collection

I Made it



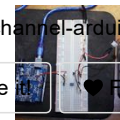
Simple, Cheap Motor Controller (/id/Simple-Cheap-Controller)



Isolating circuits from your arduino with optocouplers (/id/Isolating-circuits-from-your-arduino-with-optocouplers)



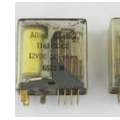Arduino smart extension cord (/id/Arduino-smart-extension-cord/) by Moose Dr



How to use any relay with your arduino the safe way (/id/How-to-use-any-relay-with-your-arduino-the-safe-way)

There are a few add-ons out there that you can buy such as power and motor shields for your Arduino. They have all the muscles in one nice package. Slap those shields on your Arduino and you are ready to control motors and other high power stuff (some soldering may be required.)

Or you can do it yourself for a fraction of the cost and double the pleasure. Enter the TIP120 and its sidekicks.

THE TIP120 DARLINGTON TRANSISTOR

The TIP120 is an NPN Power Darlington Transistor. It can be used with an Arduino to drive motors, turn lights on, and drive other high power gadgets.

The TIP120 acts as a power broker or gatekeeper between the Arduino realm and the high power realm composed of the PC fan and its battery pack. The Arduino can tell the TIP120 how much power to pass from the external battery pack to the PC fan but the Arduino does not share any of its power or share pins with the PC fan or its batteries. The TIP120 is the go in between.

The TIP120 has three pins. One is called Base, which we will connect to any of the Arduino PWM pins. Through the Base pin, the Arduino can tell the TIP120 how much power to supply to the motor from the external battery pack. That's it. The TIP120 does the heavy lifting while Arduino sits back and gives orders through one of its PWM pins to the TIP120 Base pin telling it how much power to pass to the motor. The poor TIP120 has to then pass the requested power from the external power to the motor based on Arduino's request.

THE PROJECT

In this tutorial, I will build a basic circuit in which I use an Arduino to control the speed of PC fan via the TIP120. You can take this basic circuit and replace the fan with other devices.

If you want to know more about Darlington transistors you can spend some time at Wikipedia http://en.wikipedia.org/wiki/Darlington_transistor (http://en.wikipedia.org/wiki/Darlington_transistor) It's an interesting read but you don't really need to understand it to use the TIP120. Heck I don't know what most of this stuff means.

THE SIDEKICKS

ENTER THE 1K RESISTOR & 1N4004 DIODE & 1UF CAPACITOR!

The TIP120 is a very robust item. It can handle lots of power (see specs) but the Arduino can't. So we must protect the Arduino from potential party crashers. For starters, we use a 1K Ohm resistor between the Arduino pins and the TIP120 Base pin. This is insurance against electric shorts. The TIP120 can handle 60V and 5A but I assure you the Arduino won't.

Then we have those DC motors. The internal brushes on toy/hobby DC motors generate lots of potentially harmful sparks and stray electricity that needs to be blocked. Instead of guessing which motor is safe and which is not, we simply add a \$0.20 diode and \$0.10 1uF ceramic capacitor to our circuit. Some electromechanical devices such as solenoids may require different capacitors.

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

Adding the ceramic capacitor on the + & - poles of the motor will act as a filter to the back EMF and surges generated by motor brushes, which can be harmful to your circuit.

Download

+ Collection

I Made it!

♥ Favorite

🔊 Share ▾



A small ceramic capacitor in the range of .01 to 0.1 uF is probably sufficient to offer protection from hobby DC motors. But If you are using brushless motors, such as the PC fan I am using in this tutorial, don't use a capacitor.

As for the 1N4004 diode, it allows current to pass in one direction from positive to negative but will block any stray current that tries to go in the opposite direction, which might have undesirable effects on your circuit.

Unlike resistors which allow current to flow in both directions, diodes were designed to let current pass from positive into negative, not the other way around. When you look closely at those small diodes we use in our projects, you will see a ring on one end of the diode cylinder. This tough guy can block high voltage (400V) with high current (1A). Again, no need to understand all this stuff so long as you connect the circuit properly.

I am a picture person so I have lots of pictures to help me explain my point.

PARTS

- TIP120 transistor (datasheet: <http://www.futurlec.com/Transistors/TIP120.shtml>) \$0.70
- Diode 1N4004 (datasheet: <http://www.futurlec.com/Diodes/1N4004.shtml>) \$0.20
- 1K Resistor (Brown, Black, Red, Gold) \$0.10
- 1uF ceramic capacitor to be used with hobby DC motors \$0.10
- Arduino UNO with IDE
- Breadboard
- PC fan or hobby DC motor
- 9V Alkaline or 7.2V NiMh batteries (6 X AA)
- Wires.

NOTE: I don't get commission or any perks from linking to Futurlec.com. I just like their service and prices so far.

TEST SKETCH

```
// Define which pin to be used to communicate with Base pin of TIP120
transistor
int TIP120pin = 11; //for this project, I pick Arduino's PWM pin 11
void setup()
{
  pinMode(TIP120pin, OUTPUT); // Set pin for output to control TIP120 Base pin
  analogWrite(TIP120pin, 255); // By changing values from 0 to 255 you can
  control motor speed
}

void loop()
{
}
```

CREDITS

I must thank <http://luckylarry.co.uk> for his super blog.

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

Arduino Uno controls motor with TIP120 Darlington Transistor

Download

Collection

I Made it!

Favorite

Share

Flag



We have a be nice comment policy.
Please be positive and constructive.

I Made it!

Add Images

Post Comment



SarahD25 (/member/SarahD25)

10 months ago

Reply

My circuit drives the the motor, but does not vary the speed. I wonder if its a coding problem? Heres what I wrote;

```
// Define which pin to be used to communicate with Base pin of TIP120
transistor
int TIP121pin = 11; //for this project, I pick Arduino's PWM pin 11
void setup()
{
  pinMode(TIP121pin, OUTPUT); // Set pin for output to control TIP120 Base pin
  analogWrite(TIP121pin, 255); // By changing values from 0 to 255 you can
  control motor speed
}

void loop()
{
  digitalWrite(TIP121pin, HIGH);
  analogWrite(TIP121pin, 5);
  delay(2000);
  digitalWrite(TIP121pin, HIGH);
  analogWrite(TIP121pin, 100);
  delay(2000);
  digitalWrite(TIP121pin, HIGH);
  analogWrite(TIP121pin, 255);
  delay(2000);
  digitalWrite(TIP121pin, HIGH);
  analogWrite(TIP121pin, 0);
  delay(2000);
}
```

Any ideas most welcome

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

Download

SarahD25 (/member/SarahD25) ▶ SarahD25 (/member/SarahD25)

+ Collection

Reply

Made it!

♥ Favorite

🔊 Share ▾



Please note I'm using a TIP121, I'm also using a switching mode power supply (set at 9v) and not batteries, my motor is DC 6-15v

<http://uk.rs-online.com/web/p/dc-geared-motors/0420596/>



sistemiinterattivi.abar (/member/sistemiinterattivi.abar) ▶ SarahD25

(/member/SarahD25)

a month ago

Reply

Your sketch is always setting the speed to maximum speed.

If you remove the digitalWrite(TIP121pin, HIGH) instructions it'll work!



igourlay (/member/igourlay) ▶ SarahD25 (/member/SarahD25)

Reply

10 months ago

Hey SarahD25,

So I tried your code with a different transistor but the same type and it gives me the usual behavior of a variable current flow. I would recommend removing those digitalWrite(TIP121pin, HIGH) commands because the analogWrite is all you probably need. However, the problem at hand is that your motor isn't varying its RPM so if I were to guess, the transistor might be damaged and it is acting like a short circuit.

If you have a multimeter there are tests you can do on the leads to see if it is damaged; Google can help there.

Otherwise your code is fine minus the digitalWrite(), unless they are purposefully put in there but I don't really see why. The digitalWrite() is just outputting a fraction of time of a digital high signal so ~5V (Arduino Uno) then your analogWrite() is sending periodic digital high signals (aka PWM). So long story short I don't think you need those digitalWrite() commands in this instance.

I'm new here, sorry if that was long winded.

Hope that helps!



JeffD158 (/member/JeffD158)

3 months ago

Reply

You may want to move to a MOSFET instead of a TIP-120. Runs alot cooler.

Check out: <http://sensitiveresearch.com/elec/DoNotTIP/index.html>



Franciscodr (/member/Franciscodr) made it!

3 months ago

Reply

Hi!

I made the same but to control a DC motor for a drone. Thanks! ;-)

<https://twitter.com/Franciscodr/status/837782224233717760>

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

Download

+ Collection

I Made it!

♥ Favorite

🔊 Share ▾



(<https://cdn.instructables.com/FZW/62ON/IZT6FGZ7/FZW62ONIZT6FGZ7.LARGE.jpg>)



Esan.shraideh (/member/Esan.shraideh)

2 years ago

Reply

HI

HOW I CAN RUN MOTOR IN FORWARD AND BACKWARD



lowendguru (/member/lowendguru) ▶ Esan.shraideh (/member/Esan.shraideh)

2 years ago

Reply

You should use an "H Bridge" and 2 pins of the arduino, that way you can choose the polarity. And you should turn CAPS LOCK off, keeping it on is bad Internet etiquette..



mohamedaalisher (/member/mohamedaalisher) ▶ lowendguru

(/member/lowendguru)

3 months ago

Reply

pls tell me the codes for u said



scshepard (/member/scshepard)

6 months ago

Reply

hi, many thanks; got my simple little LED output from transistor under Arduino control now. wee!




drtuto (/member/drtuto) made it!

7 months ago

Reply

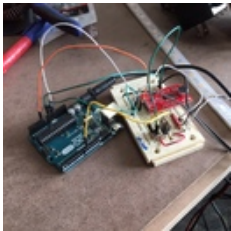Used it to control a strip of 12V LEDs and it is awesome. So a microphone board from Sparkfun controls the brightness. Thanks much...



(<https://cdn.instructables.com/F9S/3QGH/IUYD1189/F9S3QGHIUYD1189.LARGE.jpg>)



RobertV89 (/member/RobertV89)

9 months ago

Reply

I created the circuit and uploaded the sketch to my Arduino without issue, or so it seemed. My varying the analogwrite value between 0 and 250 I can change the output voltage, but I can only vary it between 5V and the 10V of my power supply. At a value of 0 it is still outputting 5V. Is that a limitation of the transistor used in this demo? If so, what do I need to look for in a transistor? I do not necessarily need it to go to zero but it would need to 'turn off' at some point.



NaveenN27 (/member/NaveenN27)

a year ago

Reply

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

can we control two directions? and can v use pwm for speed control?

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

Download

+ Collection

I Made it!

Favorite

Share



Gabrielin (/member/Gabrielin) ▸ NaveenN27 (/member/NaveenN27)

Reply

a year ago

If you want to control two directions, check out for a transistor H bridge. It is basically a circuit made of 4 transistors that allows you to choose a direction for the motor. And yes, you can use PWM for speed control. Anyway, I recommend using MOSFET transistors instead of TIP120, because the TIP ones are too old, and they usually dissipate a lot of your power, and might even overheat and stop working.



NaveenN27 (/member/NaveenN27) ▸ Gabrielin (/member/Gabrielin)

Reply

a year ago

ok , thank you so much (y)
May i know how to control the speed of the moors using mosfets as a h bridge?



JuneilS (/member/JuneilS)

a year ago

Reply

i have tried making the circuit, but instead of 9v battery, I used 12v dc from unregulated power supply. but when i measured the voltage supplied to the motor. it barely reaches 8v. i dont seem to understand it. does anyone know why does it happen?



Gabrielin (/member/Gabrielin) ▸ JuneilS (/member/JuneilS)

a year ago

Reply

TIP120 is an old and outdated transistor. For higher power applications, like yours, you would rather use a MOSFET. TIP120 will overheat and dissipate lots of your power, and might even stop working if it gets too hot.



Gabrielin (/member/Gabrielin) ▸ JuneilS (/member/JuneilS)

a year ago

Reply

TIP120 is an old and outdated transistor. For higher power applications, like yours, you would rather use a MOSFET. TIP120 will overheat and dissipate lots of your power, and might even stop working if it gets too hot.



alexandru_88 (/member/alexandru_88)

a year ago

Reply

The electrical diagram it,s not good.The N conection of the tranzistor it,s separate from P conection.



7-Factories (/member/7-Factories)

a year ago

Reply

This is great, and thank you for posting this, but do you know how to do something like this on a tiny scale? What much smaller transistor can handle this current when you need to make a tiny board for the project?



OmiW1 (/member/OmiW1)

a year ago

Reply

hello, i've already setup the circuit as shown but only different on diode 1N4007

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

the TIP120 has a problem. Only it is not spinning the motor. I used a 10k potentiometer to control the speed. I don't think the problem is from your diode or transistor so make sure you connected the sensor correctly

Download

+ Collection

I Made it!

♥ Favorite

🔊 Share ▾



CharbelE (/member/CharbelE) ▶ OmiW1 (/member/OmiW1) a year ago

Reply

hello, i did this project with TIP122 and 1N4007 and it worked great... i used a 10k potentiometer to control the speed . I don't think the problem is from your diode or transistor so make sure you connected the sensor correctly



krikkit (/member/krikkit)

a year ago

Reply

I made did this project a while ago. It worked perfectly. Then I left to do some stuff, but when I came back hours later, the TIP120 had burned the plastic around the holes in the breadboard, it was that hot. From what I understand, you're supposed to attach a heatsink to the TIP120, or better yet, just use a different transistor. I'm redoing this with a 2n7000.



Altoidian (/member/Altoidian)

a year ago

Reply

I made it and also applied a 5 v voltage regulator (xx7805) for the Arduino so I could run it from a 12 V DC wall wart unregulated. I used a Nano and hooked up the same pin numbers. My project required the motor to be on for one second and off for ten seconds to slowly rotate a wheel to reduce the RPM from 150 to just once every two minutes. It worked perfectly after I included appropriate delays in the program.

Thanks very much for your help in this instructable. I will post my project as an instructable and refer back to this project to help viewers learn how to do the motor control.



lpradhan1 (/member/lpradhan1)

a year ago

Reply

Can I use TIP122 instead of TIP120 ??



Altoidian (/member/Altoidian) ▶ lpradhan1 (/member/lpradhan1)

Reply

Yes...TIP120-122 are all NPN Darlington Transistors.

a year ago

Anytime you wonder about your transistor, look up the data sheet and it will tell you. for example, here:
<https://www.adafruit.com/datasheets/TIP120.pdf>. You will see your TIP120 listed with the TIP122.



RoarLionman (/member/RoarLionman)

a year ago

Reply

I am trying to do this with a 5VDC heating pad:
<https://www.sparkfun.com/products/11288>
(<https://www.sparkfun.com/products/11288>)

Should I still have the capacitor across the two heating pad leads?

cgalliher (/member/cgalliher)



Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

so I'm looking at the spec sheet, and it looks to me like the 2 years ago

With 3.3V outputs like on a teensy/lc? I'm googling it, but haven't come up with the right component yet. I want to address LED strings as in a costume using

teenies, in case you are wondering...

Download

+ Collection

I Made it!

♥ Favorite

🗣 Share ▾



ColinC15 (/member/ColinC15)

2 years ago

Reply

This is a great setup thank you.

Should I get a larger resistor if I were to use a large 12v battery with a drill motor?



BasmanD (/member/BasmanD)

2 years ago

Reply

if i dont have tip 120, which one can substitute it?



cheekid (/member/cheekid) ▶ BasmanD (/member/BasmanD) 2 years ago

Reply

Any NPN transistor rated for your application will do.



ahbee87844 (/member/ahbee87844) ▶ BasmanD (/member/BasmanD)

Reply

i am using this s8050 npn & it work

2 years ago



eyalasulin11 (/member/eyalasulin11)

2 years ago

Reply

i can use dc motor and don't use pc fan?



cheekid (/member/cheekid) ▶ eyalasulin11 (/member/eyalasulin11)

Reply

Yes, you can.

2 years ago



icey.hood (/member/icey.hood)

2 years ago

Reply

Does it matter if i wired the transistor directly to power and the +ve of fans to the emmitter?



cheekid (/member/cheekid) ▶ icey.hood (/member/icey.hood) 2 years ago

Reply

I'm not sure what you mean. Show a diagram and we can assist you.



SpencerD1 (/member/SpencerD1)

2 years ago

Reply

if i do all of this except put the capacitor on the motor what are the consequences?



cheekid (/member/cheekid) ▶ SpencerD1 (/member/SpencerD1)

Reply

The capacitor is there to filter nosie. Depending on your curcuit you may be fine without it. Everything will still work just not as smoothly as


2 years ago

it could work.

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

★

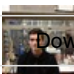

Download

2 years ago

+ Collection

Reply

I Made it!


Favorite

Share

Flag

satchelfrost (/member/satchelfrost)

Hi, I just recently built a project using the ATtiny85 (rated I think somewhere between 2 to 5V). The project uses a simple code with a potentiometer to control the speed of a DC motor. Wouldn't you know it, after spending a lifetime soldering, the motor doesn't have enough torque for my needs. I had put a 5V voltage regulator in the circuit with the IC to prevent frying the thing, but now it's looking like I need a more powerful DC motor. Do you think this TIP120 will solve my problems?




cheekid (/member/cheekid)

▶ satchelfrost (/member/satchelfrost)

2 years ago

Reply

Your project requires a geared motor. The TIP120 will not solve this problem.




dfshk (/member/dfshk)

2 years ago

Reply

Would this also work with a 3.3V Arduino Pro?




cheekid (/member/cheekid)

▶ dfshk (/member/dfshk)

2 years ago

Reply

Yes, bare in mind the Arduino is not handling the voltage or amp draw. The Arduino like the posted stated is only there to give orders. Your connected device and power source are operated independently. The Arduino is the boss. Make sure you understand the basics before doing this project. If you start with less you'll be much better off because you'll have a greater understanding.




SIM-Tech (/member/SIM-Tech)

2 years ago


Reply

this is so stupid like a 12V fan ? really why wud anyone need to do this with a MCU ? is a over kill just stick a 9V battery to it with a switch thats it,,, NOW if your going to include some IF statements while adding some sort of sensor NOW this is a reason to use a MCU but as a stand along is just a waste of time, even a DC motor could have suffice with just a 9V a resistor and a TIP120??? hell no a Voltage regulator 7805 would have done the trick while saving voltage obvs by regulating it no need for a mcu

i included one of my mini humanoid robots and this is worth a ATTINY MCU for all this motor i have used here



(https://cdn.instructables.com/FDR/GW9U/IC5C63EY/FDRGW9UIC5C63EY.LARGE.jpg)



cheekid (/member/cheekid)

▶ SIM-Tech (/member/SIM-Tech)

2 years ago

Reply

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

Of course it isn't needed. He is demonstrating how to use the transistor with an Arduino nothing more. So I don't have to make something like this. But the basic setup will remain the same. It's all about building blocks by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/) Switch on a led, now switch on led with a transistor, now switch on an led with a transistor through a relay. Those basic steps with the addition of other components will allow the user to control many things. So is it really "stupid" Nope not at all.

Download

I Made it!

Favorite

Share



vipul.swamy (/member/vipul.swamy)

2 years ago

Reply

Wow!! thank you...



LiviuC (/member/LiviuC)

2 years ago

Reply

Hello there.

I have some issues with this project: i used all the specified parts but instead of TIP120 i have used TIP121 and instead of 1N4004 i used 1n4007.

I uploaded that program but my fan start rotatig continuously ,and if i pull de pin 11 from Arduino nothing happens.i thought it was supposed to stop .

I used that parts because i couldn't find the desired ones .

I want to rotate my fan at a specific moment.

Any ideas? thx



ahbee87844 (/member/ahbee87844) ▶ LiviuC (/member/LiviuC)

Reply

2 years ago

analogWrite(TIP120pin, 255); fan on

analogWrite(TIP120pin, 0); fan off



patrick.roncagliolo (/member/patrick.roncagliolo) ▶ LiviuC (/member/LiviuC)

2 years ago

Reply

Obviously, that sketch sets a specific PWM value. So you won't see any variation in the fan rotating speed. Try with a loop ranging from 0 to 255 and back again to 0, with some millis between each cycle.



ahbee87844 (/member/ahbee87844) made it!

2 years ago

Reply

Hi techbitar, thank for the guide and it very simple to follow your procedure. Manage to get the project running in less than 30 mins.

1 question here : i had some voltage & current taken down. Volt on 1k ohm is 3.33v & current 3.33ma. Can you share with me why is the 1K Ohm resistor chosen & not other value?



(<https://cdn.instructables.com/FIG/X23Q/1AXRO1SD/FIGX23Q1AXRO1SD.LARGE.jpg>)

Use Arduino With TIP120 Transistor to Control Motors and High Power Devices

PrashantD1 (/member/PrashantD1/)

2 years ago

Reply

by techbitar (/member/techbitar/) in arduino (/tag/type-id/category-technology/channel-arduino/)

Awesome, very well explained, the analogy is just pure icing for beginners.

Thank you for the instruct-able.

+ Collection

I Made it!

Favorite

Share



More Comments

FEATURED CHANNELS

Woodworking
(/tag/type-id/category-workshop/channel-craft/channel-woodworking/)

Paper
(/tag/type-id/category-paper/)

Kitchen Hacks
(/tag/type-id/keyword-kitchen%20hacks/?sort=FAVORITES)

Puzzles
(/tag/type-id/category-play/channel-puzzles/)


Laser Cutting
(/tag/type-id/category-workshop/channel-astronomy/?sort=FAVORITES)

Space
(/tag/type-id/keyword-home/channel-technology/channel-craft/channel-sewing/)

Homesteading
(/tag/type-id/category-3D-Printing/)

3D Printing
(/tag/type-id/category-craft/channel-sewing/)

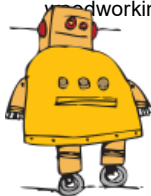Sewing
(/tag/type-id/category-craft/channel-sewing/)



Newsletter

Let your inbox help you discover our best projects, classes, and contests. Instructables will help you learn how to make anything!

enter email

I'm in!

About Us

Who We Are (/about/)

Advertise (/advertise/)

Contact (/about/contact.jsp)

Jobs (/community/Positions-available-at-Instructables/)

Help (/id/how-to-write-a-great-instructable/)

Resources

For Teachers (/teachers/)

Residency Program (/pier9residency)

Gift Premium Account (/account/give?sourcea=footer)

Forums (/community/)

Answers (/tag/type-question/?sort=RECENT)

Sitemap (/sitemap/)

Find Us

Facebook (<http://www.facebook.com/instructables>)

Youtube (<http://www.youtube.com/user/instructablestv>)

Twitter (<http://www.twitter.com/instructables>)

Pinterest (<http://www.pinterest.com/instructables>)

Google+ (<https://plus.google.com/+instructables>)

Terms of Service (<http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21959721>) |

Privacy Statement (<http://usa.autodesk.com/adsk/servlet/item?siteID=123112&id=21292079>) |

Legal Notices & Trademarks (<http://usa.autodesk.com/legal-notice-trademarks/>) | Mobile Site (<https://www.instructables.com>)



(<http://usa.autodesk.com/adsk/servlet/pc/index?id=20781545&siteID=123112>)

© 2016 Autodesk, Inc.